

EENG 5560 HW 2 Report

Name: Sanjay Bhaskar

Due: 02/08/2024

Table of Contents

Design	3
Block diagrams	3
Overall design	3
Subcomponents	5
Design explanation.....	6
Functionality	6
Results.....	8
Generated Schematic	8
Waveforms.....	11
Table/Calculations	14
Overall Design	14
Subcomponent test cases.....	15
References.....	17

*

Design

Block diagrams.

Overall design

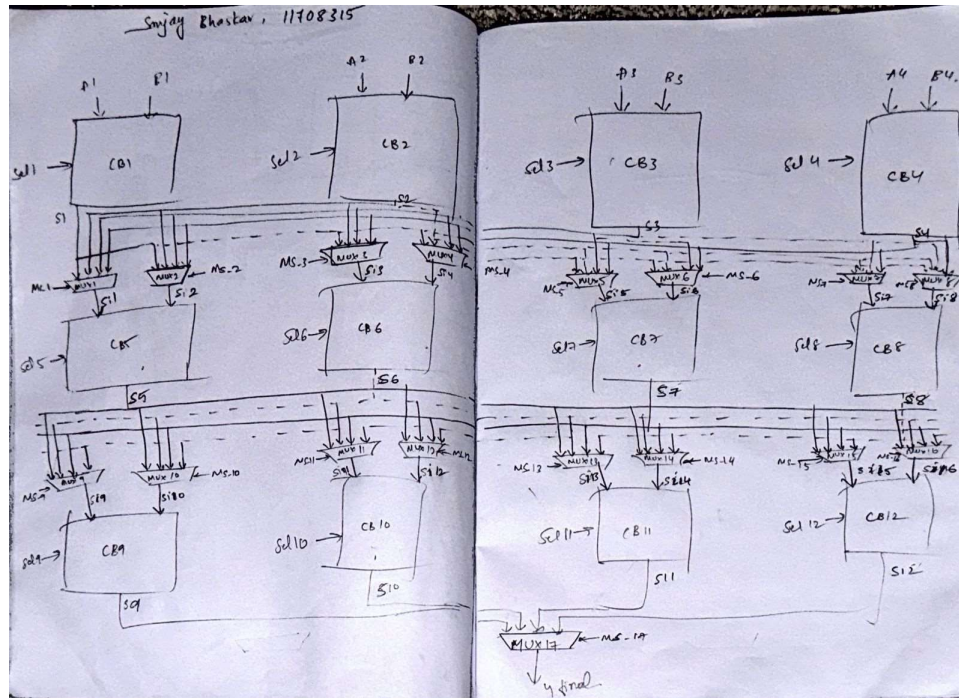


Figure 1- top module: Overall Design Block Diagram

- Overall Component: ASSIGNMENT_2[4X3]
- Overall ports for case_1:
 - Inputs:
 - A1: 6 bits
 - B1: 6 bits
 - A2: 6 bits
 - B2: 6 bits
 - A3: 6 bits
 - B3: 6 bits
 - A4: 6 bits
 - B4: 6 bits
 - Outputs:
 - YFINAL: 6 bits
- Subcomponents:
 - 1.COMPUTATIONAL BLOCK (CB1, CB2, CB3, CB4, CB5,CB7,CB10)—Rotate Right, Subtraction, NAND, XOR, OR, ADD and Greater Than.

2.MULTIPLEXER (Mux1, Mux2, Mux5, Mux6, Mux11, Mux12, Mux17)-4:1

- Necessary intermediate signals:
 - S1, S2, S3, S4, S5, S7, S10.
 - Sel_1, Sel_2, Sel_3, Sel_4, Sel_5, Sel_7, Sel_10—Each Computational Block
 - Ms_1, Ms_2, Ms_5, Ms_6, Ms_11, Ms_12, Ms_17—Each Mux

Parameters: d_w – data width (for inputs and outputs)

Input ports and intermediate signals:

Port name	Bit width	Purpose
A1, B1,A2,B2,A3,B3,A4,B4	d_w = 6	Data inputs
Sel_1, Sel_2, Sel_3, Sel_4, Sel_5, Sel_6, Sel_7, Sel_8, Sel_9, Sel_10, Sel_11, Sel_12.	w = 5	Selection line, selects data input to send to output for Computational Units
Ms_1, Ms_2, Ms_3, Ms_4, Ms_5, Ms_6, Ms_7, Ms_8, Ms_9, Ms_10, Ms_11, Ms_12, Ms_13, Ms_14, Ms_15, Ms_16, Ms_17.	w = 2	Selection line, selects data input to send to output for Mux's
S1, S2,S3,S4,S5,S6,S7,S8,S9,S10, S11,S12	w = 6	Signal lines i.e., Output from CU's
Si1, Si2, Si3, Si4, Si5, Si6, Si7, Si8, Si9, Si10, Si11, Si12, Si13, Si14, Si15, Si16	w = 6	Signal lines i.e., Output from MUX's

Output ports:

Port name	Bit width	Purpose
YFINAL	d_w = 6	Data output

- Overall ports for case_2:
 - Inputs:
 - A1: 6 bits
 - B1: 6 bits
 - A2: 6 bits
 - B2: 6 bits
 - A3: 6 bits
 - B3: 6 bits
 - A4: 6 bits
 - B4: 6 bits
 - Outputs:
 - YFINAL: 6 bits
- Subcomponents:
 - 1.COMPUTATIONAL BLOCK (CB1, CB2, CB3, CB4, CB6, CB8, CB11)—AND, LSL, LSR, MULT, ROL, NE, OR.
 - 2.MULTIPLEXER (Mux3, Mux4, Mux7, Mux8, Mux13, Mux14, Mux17)-4:1

- Necessary intermediate signals:
 - S1, S2, S3, S4, S6, S8, S11.
 - Sel_1, Sel_2, Sel_3, Sel_4, Sel_6, Sel_8, Sel_11—Each Computational Block
 - Ms_3, Ms_4, Ms_7, Ms_8, Ms_13, Ms_14, Ms_17—Each Mux

Subcomponents

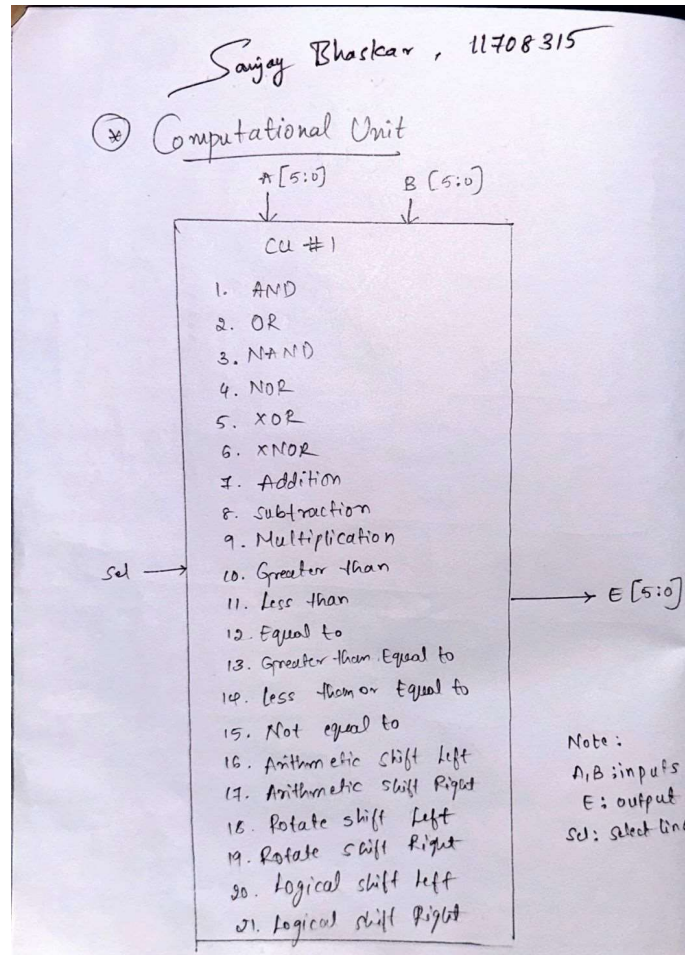


Figure 2- Subcomponent: Computational Unit Block Diagram

Subcomponent: Computational Unit Block Diagram

Input ports:

Port name	Bit width	Purpose
A,B	d_w = 6	Data inputs
Sel	5	Select line, selects which of the 2 data inputs to send to data output

Output ports:

Port name	Bit width	Purpose
E	d_w = 6	Data output

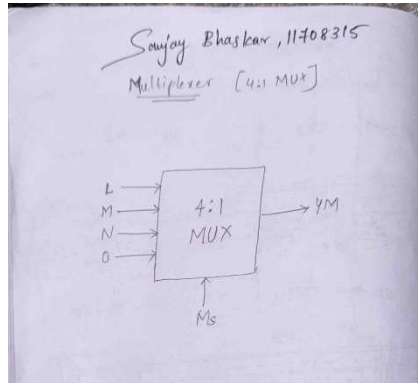


Figure 3- Subcomponent: 4:1 MUX Block Diagram

Subcomponent: 4x1 mux

Input ports:

Port name	Bit width	Purpose
L,M,N,O	d_w = 6	Data inputs
Ms	2	Select line, Selects one of the following operations out of 4.

Output ports:

Port name	Bit width	Purpose
YM	d_w = 6	Data output

Design Explanation

Functionality

Behavioral design functionality explanation: To form a Top-level Design there are few steps to follow. First we need to write a code for Computational Unit and write the test bench for CU and verify all 21 operations are working properly. Verify the output waveform with the Expected calculations. Then write a code for MUX which is required to connect CUs in consecutive levels because we need to connect the CUs in matrix format. So, write the test bench for Mux and verify with the expected output.

In this case Mux expected output Truth Table is b

Select input	Resulting output
00	L
01	M
10	N
11	O

In this case 4:1 Mux is used which has 2 bits select line. Combination of the 2 bits select line is responsible for choosing the appropriate inputs.

If combination is resulting in “00” then resulting output will be 1st input i.e., L.

If combination is resulting in “01” then resulting output will be 2nd input i.e., M.

If combination is resulting in “10” then resulting output will be 3rd input i.e., N.

If combination is resulting in “11” then resulting output will be 4th input i.e., O.

Now, Computational Units outputs can be connected to Mux and Output of Mux can be connected to Computational Units.

After this write a code to connect Computations units and design an Overall Design i.e., 4X3 computational Unit.

All the computational units that were designed is arranged in a matrix(3X4) format and are named accordingly (1,1), (1,2), (1,3), (1,4), (2,1), (2,2), (2,3), (2,4), (3,1), (3,2), (3,3), (3,4).

In Case 1: The very first row CUs in the matrix is connected to two of the CUs in the second row respectively (2,1) and (2,3) via MUX [4:1]. Since the direct connection of CUs are not very efficient, Connection of required CUs are done with the help of MUX.

There is a total of 17 MUX used for building an overall design. Precisely in the above case a total of 7 Muxes are used to connect CUs per the given case: 1. Mux 1, 2, 5, 6 are used for connecting Cu's in row 1 and row 2 whereas Mux 11 and 12 are used for connecting row 2 and 3 respectively. The final output is taken from CU (3,2) which is in turn connected to Mux 17.

Results

Generated Schematics

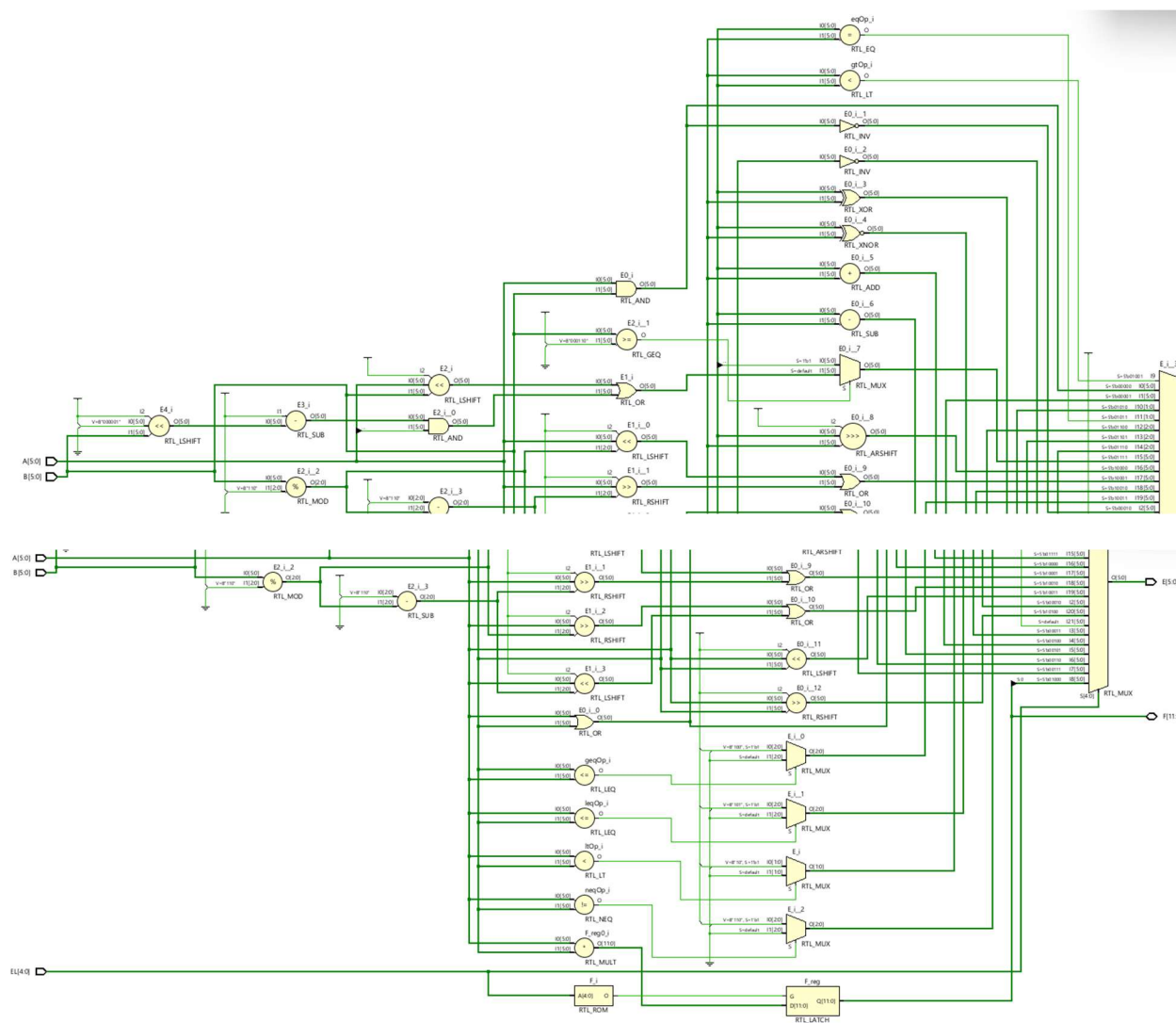


Figure 4 – Computational Unit RTL Schematic.

This is the RTL Schematic of Computational Unit.

All 21 operations are listed in this RTL Schematic and Due to picture is big I have added 2 pictures such as first part and second part.

All the 21 operations is listed in this RTL Schematic respectively, Whereas,

RTL Mux is the component the system is using to combine all 21 inputs and give only one output.

As there are 21 operations, we need at least 5 bit select line in binary.

- 1) If we select “00000” from the select line, then the output will be AND operation.
- 2) If we select “00001” from the select line, then the output will be OR operation.
- 3) If we select “00010” from the select line, then the output will be NAND operation.
- 4) If we select “00011” from the select line, then the output will be NOR operation.
- 5) If we select “00100” from the select line, then the output will be XOR operation.
- 6) If we select “00101” from the select line, then the output will be XNOR operation.
- 7) If we select “00110” from the select line, then the output will be ADD operation.
- 8) If we select “00111” from the select line, then the output will be SUB operation.
- 9) If we select “01000” from the select line, then the output will be MUL operation.
- 10) If we select “01001” from the select line, then the output will be GT operation.
- 11) If we select “01010” from the select line, then the output will be LT operation.
- 12) If we select “01011” from the select line, then the output will be EQ operation.
- 13) If we select “01100” from the select line, then the output will be GTE operation.
- 14) If we select “01101” from the select line, then the output will be LTE operation.
- 15) If we select “01110” from the select line, then the output will be NEQ operation.
- 16) If we select “01111” from the select line, then the output will be Arithmetic Shift Left operation.
- 17) If we select “10000” from the select line, then the output will be Arithmetic Shift Right operation.
- 18) If we select “10001” from the select line, then the output will be Rotate Shift Left operation.
- 19) If we select “10010” from the select line, then the output will be Rotate Shift Right operation.
- 20) If we select “10011” from the select line, then the output will be Logical Shift Left operation.
- 21) If we select “10100” from the select line, then the output will be Logical Shift Right operation.

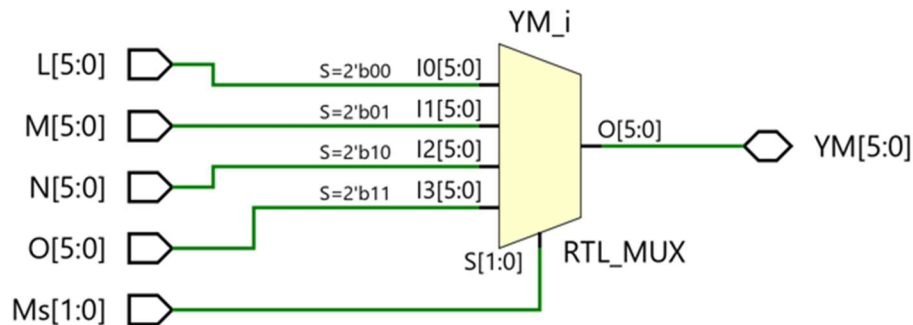


Figure 5 - 4x1 mux RTL schematic.

This is the RTL Schematic of Mux.

As per the above circuit diagram we can see RTL schematic diagram is same and naming is also same so that it will be easy to analyze and understanding the module.

L,M,N,O is the inputs taken in handwritten ckt diagram and it's same in the RTL schematic too. Ms is the Mux Select line, and YM is the output.

- 1) L[5:0] is mapped with L
- 2) M[5:0] is mapped with M
- 3) N[5:0] is mapped with N
- 4) O[5:0] is mapped with O

- 5) Ms[1:0] is mapped with Ms
- 6) O[5:0] is mapped with O

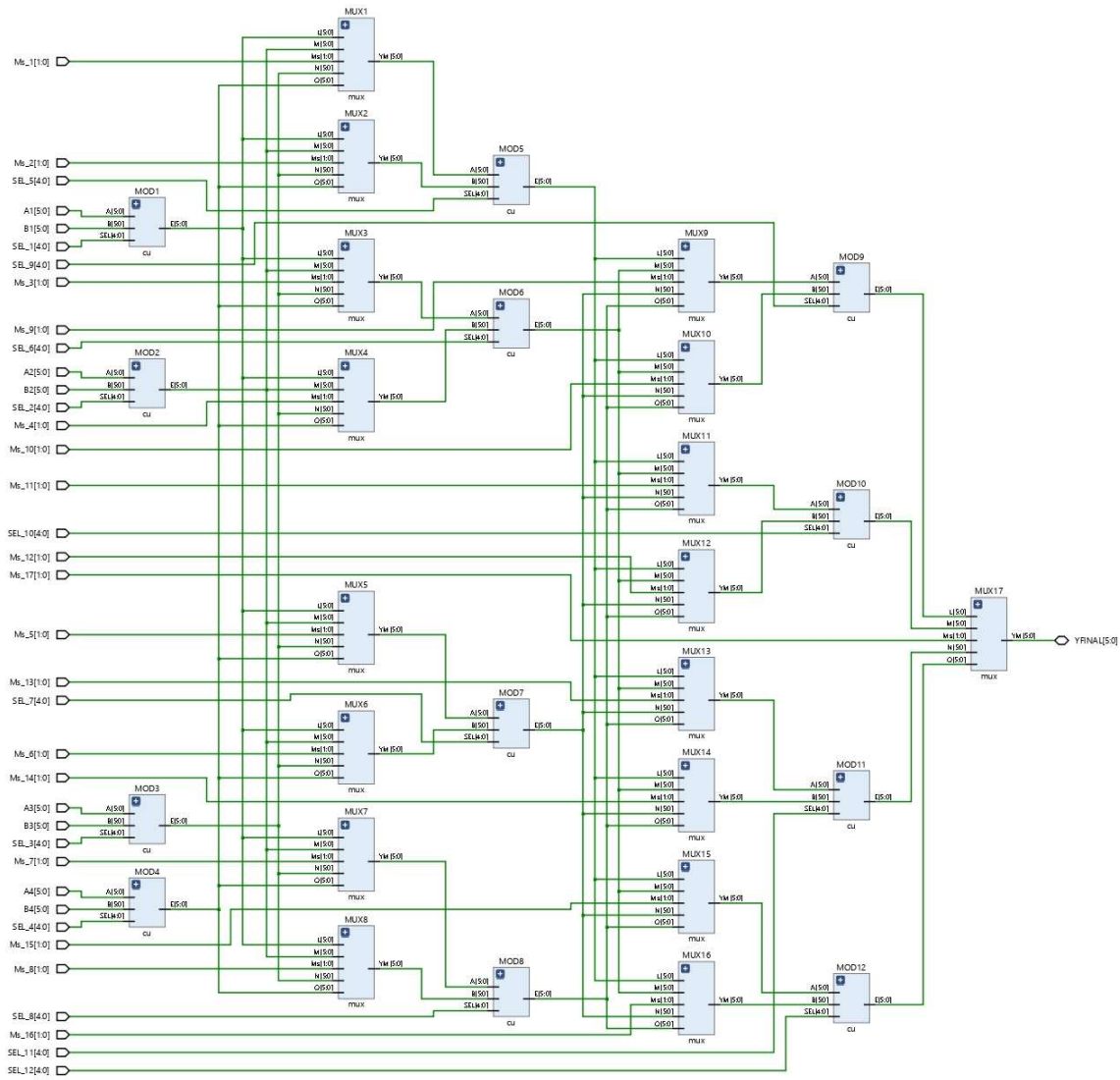


Figure 6 – Overall Design RTL schematic.

In the generated schematic, there are 4:1 muxes receiving the 6 bit data from Computational Units from row 1 to row 2 and row 2 to row 3, overall data inputs and using the select lines of Cus and select line of muxes we can connect any of the Cu in 1st row to the any of the Cu in the 2nd row and so on. The outputs of the 4x1 muxes are fed as inputs to the 2nd row CUs. The output of the 2nd row CUs is connected to again muxes as input and output of the mux is connected to Cu in the third row. This is effective connections where user can modify the path any time with any of the operation. This Behavior of output matches that of our design.

Waveforms

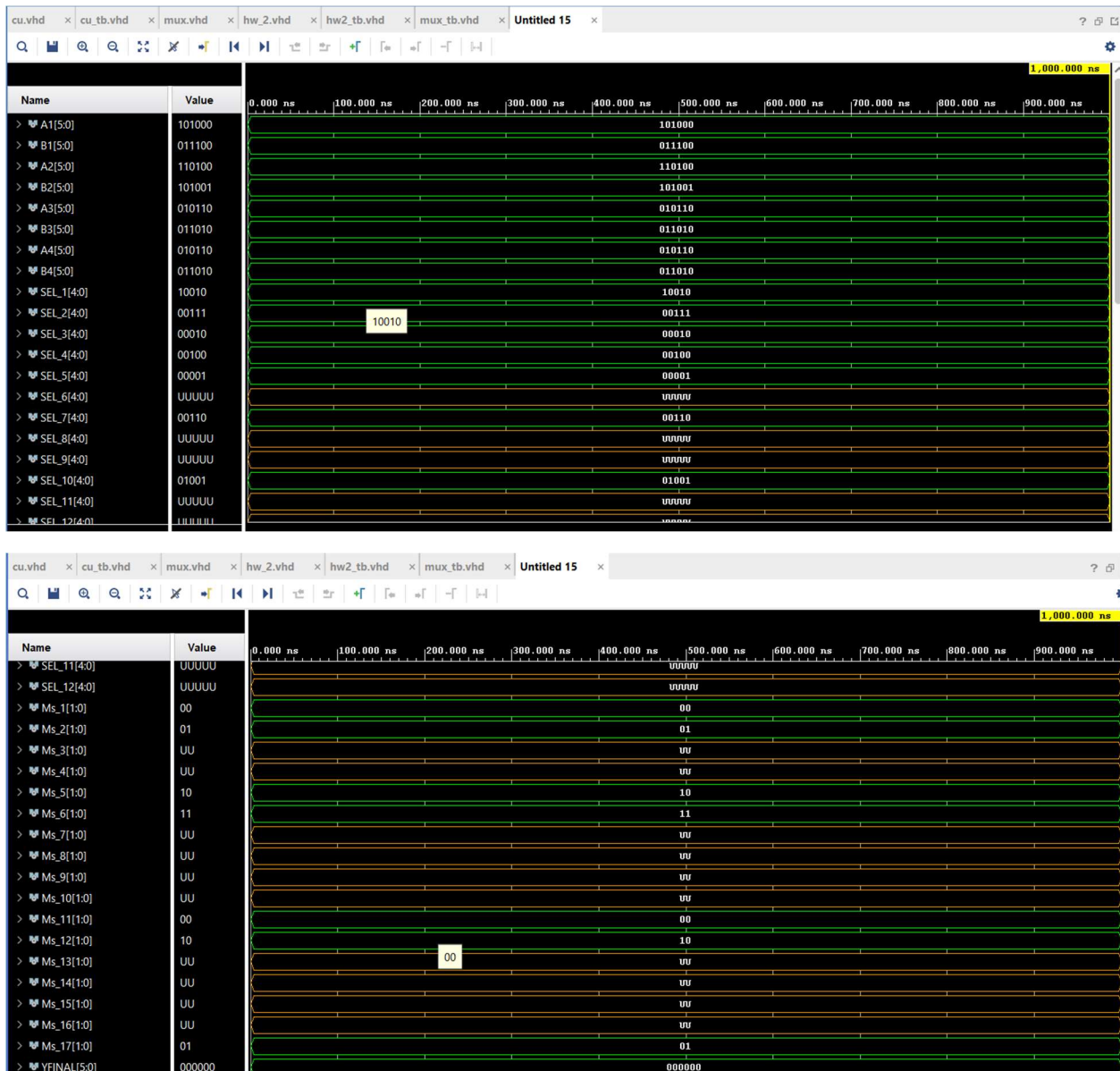


Figure 7 – Overall Waveforms for Case 1

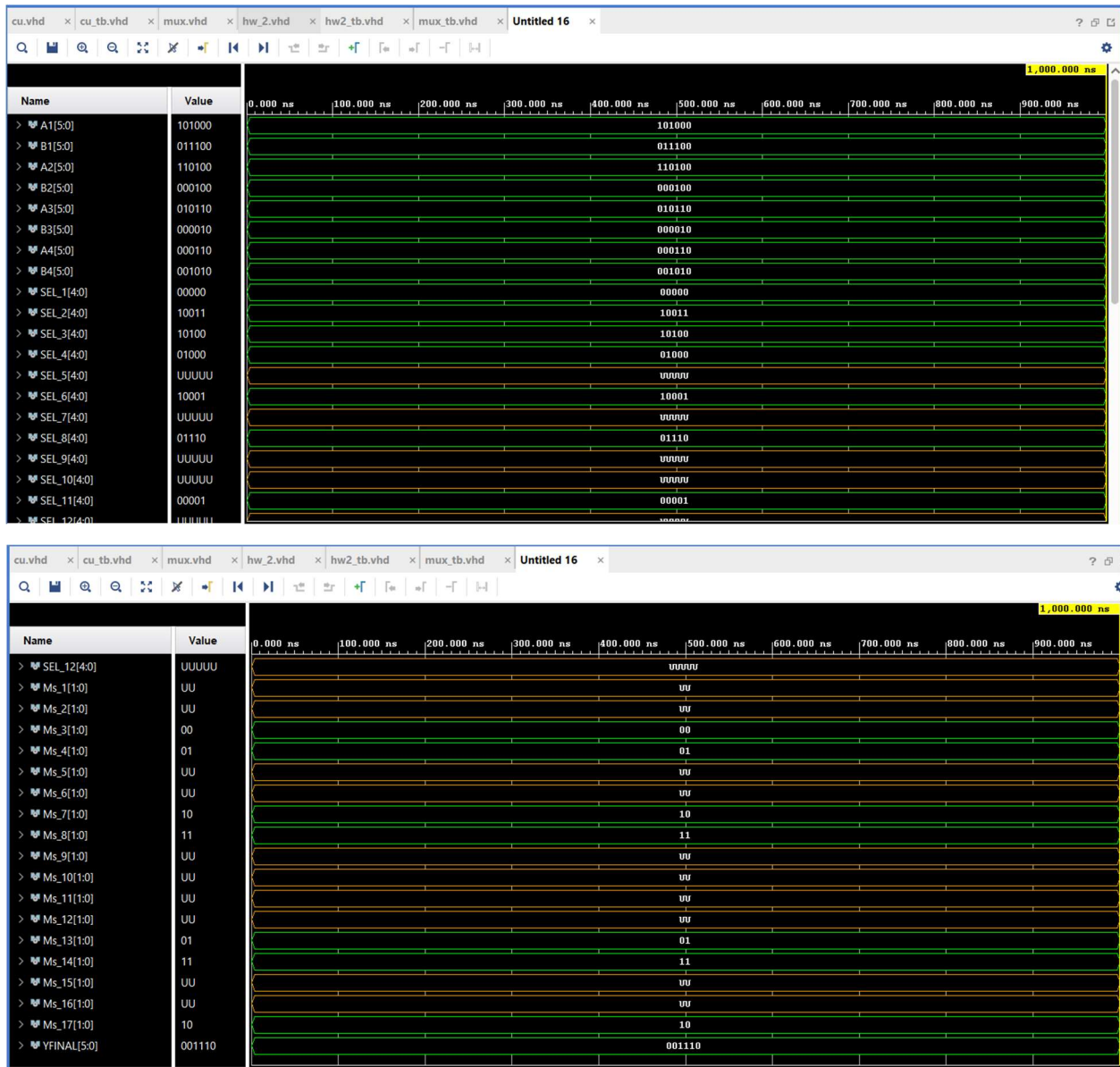


Figure 8 – Overall Waveforms for Case 2

Combinational Unit Waveforms.

 


Figure 9 – Combinational Unit Waveform part 1

> A[5:0]	111001	111001	110110	111001	110110	111001	110110	111001	110110	111001	110110	111001	110110	111001	...
> B[5:0]	110101	110101	101001	110101	101001	110101	101001	110101	101001	110101	101001	110101	101001	110101	...
> SEL[4:0]	01000	00110	00111	00111	01000	01001	01010	01011	01100						
> E[5:0]	100110	101110	011111	000100	001101	100110	001101	000001	000000	000100					

Figure 10 – Combinational Unit Waveform part 2

Name	Value	670.000 ns	680.000 ns	690.000 ns	700.000 ns	710.000 ns	720.000 ns	730.000 ns	740.000 ns	750.000 ns	760.000 ns	770.000 ns	780.000 ns	790.000 ns
> A[5:0]	111001	1...	110110	111001	110110	111001	110110	111001	110110	111001	110110	111001	110110	111001
> B[5:0]	110101	1...	101001	110101	101001	110101	101001	110101	101001	110101	101001	110101	101001	110101
> SEL[4:0]	01000	01100	01101	01101	01110	01111	10000	10001	10010	10011	10011	10011	10011	10011
> E[5:0]	100110	000100	000000	000110	000110	111111	000000	111111	111100	011011	110011	101101	101101	101101

Figure 11 – Combinational Unit Waveform part 3

Name	Value	780.000 ns	790.000 ns	800.000 ns	810.000 ns	820.000 ns	830.000 ns	840.000 ns	850.000 ns	860.000 ns	870.000 ns	880.000 ns	890.000 ns	900.000 ns
> A[5:0]	111001	111001	110110	111001	110110	111001	110110	111001	110110	111001	110110	111001	110110	111001
> B[5:0]	110101	110101	101001	000010	101001	110101	101001	110101	101001	110101	101001	110101	101001	110101
> SEL[4:0]	01000	10010	10011	10011	10100	10100	00000	00001	00001	00001	00010	00011	00011	00011
> E[5:0]	100110	110011	101101	100100	000000	110001	100000	111101	111111	001110	011111	011111	000010	000010

Figure 12 – Combinational Unit Waveform part 4

4:1 Mux Waveform.

cu.vhd | cu_tb.vhd | mux.vhd | hw_2.vhd | hw2_tb.vhd | mux_tb.vhd | Untitled 18

Figure 13 – 4:1 Mux Waveform

Table/Calculations

Overall Design

Test Case 1 (0ns to 10ns):

CU#	SourceA	SourceB	A	B	Oper	Calculated Op	Simulated Op	Match
CU1	A1	B1	101000	011100	ROR	000001	000001	Yes
CU2	A2	B2	110100	101001	SUB	011111	011111	Yes
CU3	A3	B3	010110	011010	NAND	101101	101101	Yes
CU4	A4	B4	010110	011010	XOR	001100	001100	Yes
CU5	Si1	Si2	000001	011111	OR	011111	011111	Yes
CU7	Si5	Si6	101101	001100	ADD	111001	111001	Yes
CU10	Si11	Si12	011111	111001	GT	000000	000000	Yes

Test Case 2 (10ns to 20ns):

CU#	SourceA	SourceB	A	B	Oper	Calculated Op	Simulated Op	Match
CU1	A1	B1	101000	011100	AND	001000	001000	Yes
CU2	A2	B2	110100	000100	LSL	000000	000000	Yes
CU3	A3	B3	010110	000010	LSR	000101	000101	Yes
CU4	A4	B4	000110	001010	MULT	000110	000110	Yes
CU5	Si3	Si4	001000	000000	ROL	001000	001000	Yes
CU7	Si7	Si8	000101	000110	NE	000110	000110	Yes
CU10	Si13	Si14	001000	000110	OR	001110	001110	Yes

Explanation:

As can be seen by the table, the waveform output values for both test cases match the calculated values. This means the design works properly.

Case 1 manual calculations and waveform values matches exactly the same.

Subcomponent test cases

Test Case 0ns to 10ns:

Sl no.	A	B	Oper	Calculated Op	Simulated Op	Match
1	111001	110101	AND (00000)	110001	110001	Yes
2	111001	110101	OR (00001)	111101	111101	Yes
3	111001	110101	NAND(00010)	001110	001110	Yes
4	111001	110101	NOR(00011)	000010	000010	Yes
5	111001	110101	XOR(00100)	001100	001100	Yes
6	111001	110101	XNOR(00101)	110011	110011	Yes
7	111001	110101	ADD(00110)	101110	101110	Yes
8	111001	110101	SUB(00111)	000100	000100	Yes
9	111001	110101	MUL(01000)	100110	100110	Yes
10	111001	110101	GT(01001)	000001	000001	Yes
11	111001	110101	LT(01010)	000000	000000	Yes
12	111001	110101	EQ(01011)	000000	000000	Yes
13	111001	110101	GTE(01100)	000100	000100	Yes
14	111001	110101	LTE(01101)	000000	000000	Yes
15	111001	110101	NEQ(01110)	000110	000110	Yes
16	111001	110101	SLA(01111)	111111	111111	Yes
17	111001	110101	SRA(10000)	111111	111111	Yes
18	111001	110101	ROL(10001)	111100	111100	Yes
19	111001	110101	ROR(10010)	110011	110011	Yes
20	111001	110101	SLL(10011)	100100	100100	Yes
21	111001	110101	SRL(10101)	000000	000000	Yes

Test Case 2 (*5ns to 10ns*):

Sl no.	A	B	Oper	Calculated Op	Simulated Op	Match
1	110110	101001	AND (00000)	100000	100000	Yes
2	110110	101001	OR (00001)	111111	111111	Yes
3	110110	101001	NAND(00010)	011111	011111	Yes
4	110110	101001	NOR(00011)	000000	000000	Yes
5	110110	101001	XOR(00100)	011111	011111	Yes
6	110110	101001	XNOR(00101)	100000	100000	Yes
7	110110	101001	ADD(00110)	011111	011111	Yes
8	110110	101001	SUB(00111)	001101	001101	Yes
9	110110	101001	MUL(01000)	001101	001101	Yes
10	110110	101001	GT(01001)	000001	000001	Yes
11	110110	101001	LT(01010)	000000	000000	Yes
12	110110	101001	EQ(01011)	000000	000000	Yes
13	110110	101001	GTE(01100)	000100	000100	Yes
14	110110	101001	LTE(01101)	000000	000000	Yes
15	110110	101001	NEQ(01110)	000110	000110	Yes
16	110110	101001	SLA(01111)	000000	000000	Yes
17	110110	101001	SRA(10000)	111111	111111	Yes
18	110110	101001	ROL(10001)	011011	011011	Yes
19	110110	101001	ROR(10010)	101101	101101	Yes
20	110110	101001	SLL(10011)	000000	000000	Yes
21	110110	101001	SRL(10101)	000000	000000	Yes

References

Referred Files from Canvas.

Manual Calculations.

Saijay Bhaskar 11708315

Case (i)

$$\begin{array}{l} A1 = 101000 \\ B1 = 011100 \end{array} \quad (ROR)$$

$$B1 = 28$$

28 time Rotate Right.

$$O/p \Rightarrow 000001 \rightarrow \underline{S11}$$

$$\begin{array}{l} A2 = 110100 \\ B2 = 101001 \end{array} \quad (SUB)$$

~~000001~~

$$011111 \rightarrow \underline{S12}$$

$$\begin{array}{l} A3 = 010110 \\ B3 = 011010 \end{array} \quad (NAND)$$

$$101101 \rightarrow \underline{S15}$$

$$A4 = 010110$$

$$B4 = 011010$$

$$001100 \rightarrow \underline{S16}$$

S_{i1} : 000001 (OR)

S_{i2} : 011111

011111 → S_{i11}

S_{i2} ← 000100

S_{i5} : 101101 (Add)

S_{i6} : 001100

111001 → S_{i12}

S_{i11} : 011111

S_{i12} : 111001

S_{i11} > S_{i12}

Condition doesn't

satisfy

So Y_{final} = 000000

A4: 000110
B4: 001010 (MUL)

000110 → S18

S13: 001000 (ROL)

S14: 000000

001000 → S13

S17: 000101 (NE)

S18: 000110

Condition Satisfied

As per CU Code the NE o/p will be

000110 → S14

S13 = 001000 (OK)

S14 = 000110

001110 → 4 Final

Case-2 waveform & manual calculations Satisfied.

Case-2 :

A1: 101000 (AND)

B1: 011100

001000 \rightarrow Si3


A2: 110100

B2: 000100

LSL

B2 = 4 in decimal.

Shift A by 4 times

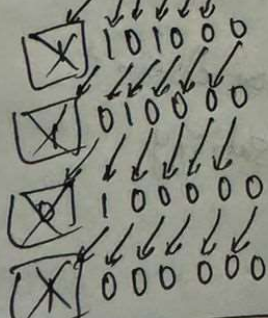110100

 101000
 010000
 100000
 000000 \rightarrow 000000 \rightarrow Si4

A3: 010110 (LSR)

B3: 000010

Shift B Right by 2 times B3 = 2 in decimal

000101 \rightarrow Si5